

# CSC258: Intro to Digital Logic



Instructors: Steve Engels, [sengels@cs.toronto.edu](mailto:sengels@cs.toronto.edu)  
Sajad Shirali-Shahreza, [shirali@cs.toronto.edu](mailto:shirali@cs.toronto.edu)

# CSC258 Course Details

- Course Goals:
  - Understand the underlying architecture of computer systems.
  - Learn how to use this architecture to store data and create behaviour.
  - Use the principles of hardware design to create digital logic solutions to given problems.



# CSC258 Course Details

- Lectures / tutorials
- Labs (28%):
  - 7 total (4% each)
  - Must complete pre-lab exercises ahead of time.
- Project (14%):
  - Large, cool digital creation.
  - Proposal and 3 demos.
- Exams:
  - Midterm (18%) – Feb 28<sup>th</sup>.
  - Final exam (40%)
    - must get 40% to pass the course.

Let the learning begin



# Why take CSC258?

- To understand computers better!
  1. How does a computer store "false" or "true" in memory?
  2. Why is there a maximum value for an `int`?
  3. Where do the operators "and", "or" and "not" come from?
  4. What actually happens when you press `Ctrl-Alt-Delete` on your keyboard?
  5. What happens when a Java or C program is compiled?

# CSC258 has the answers!

- Computers are physical things, therefore they have certain behaviours and limitations:
  - Data values are finite.
  - All data is stored as ones and zeroes at some level.
  - Many high-level operations depend on low-level ones.
- The way computers are today take their origins from how computers were created in the past.



# Example #1: Booleans

- How are boolean values stored?
- Example: `if` statements:

```
if x:  
    print 'Hello World'  
    # what values can x have  
    # that make this happen?
```

- What if `x` is a boolean?
- What if `x` is an int?
- What if `x` is a string?



All comes down to  
hardware in the end!

Text

## Example #2: Integers

- How are integers stored?

- Again, as ones and zeroes.

Decimal → 1234 → 0011000000111001 Binary


- How many values can integers have?

- This can vary based on language and architecture, but generally integers have  $2^{32}$  different values.
  - Signed integers: range from  $-2^{31}$  to  $2^{31}-1$
  - Unsigned integers: range from 0 to  $2^{32}-1$
  - Different ranges for long, short and byte.


 
# Programming hardware

- Computers do on the hardware level what programs do on the software level.



- In CSC258, designing circuits follows many of the the same ideas behind creating boolean logic in Python or Java.



# Programming parallels


## Python/Java

- Boolean variables
- Boolean operations (and, or, not, etc)
- Integers, doubles, chars
- Addition, subtraction, multiplication
- Storing values
- Executing instructions

## Computer hardware

- High and low wire values
- Logic gates (AND, OR, NOT, etc)
- Registers
- Adder circuits, multiplier circuits
- Memory
- Processors

# What you already know

 

# Programming from CSC148


- Need to have basic programming literacy.
- For CSC258, be prepared to let that all go.
  - Verilog → specification language
  - Assembly → low-level programming
- Trying to connect these languages to CSC148 will only hold you back.
  - Practice practice practice

# Logic from CSC165

- What you may not realize, is that you already know how some of the basics of logic gates.
- Example: Create an expression that is true if the variables A and B are true, or C and D are true.





$$G = A \ \& \ B \ | \ C \ \& \ D$$

 - Now create a circuit that does the same thing:



   
 
# Gates = Boolean logic

- If you know how to create simple logical expressions, you already know the basics of putting logic gates together to form simple circuits.
- Just need to know which logic operations are represented by which gate!





XOR

# AND Gates

  

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1



# OR Gates

  

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1





# NOT Gates

  

A	Y
0	1
1	0

# XOR Gates

either but not both inputs are high

  

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0



# Bill Gates



- ...ha ha...moving on....



# NAND Gates

AND gate followed by a NOT gate

  



A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

# NOR Gates

  

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

# Buffer

  


A	Y
0	0
1	1
 
# Creating complex circuits

- Creating circuit logic is the same as working with boolean logic in Python, C or Java:

```
Y = (!A and !B and !C) or (!A and  
    B and C) or (A and B and C)
```



# What you might not know yet







# Thinking in hardware

- CSC258 is very, very different.
- Unlike software, CSC258 is not about creating programs and algorithms, but rather devices and machines.
  - Very important concept to grasp early in this course!
  - Need to understand what certain terms mean in the context of hardware.



  
# What is “true” and “false”?

- Once you know the logical operation a circuit performs, all that's left is supplying the input values.
  - How do we represent boolean values like “true” and “false”?
- In hardware, “true” and “false” refers to the electrical voltage values on the wires.
  - Zero: little to no voltage at that point.
  - One: typically a voltage difference of 5 **volts**, relative to the ground.


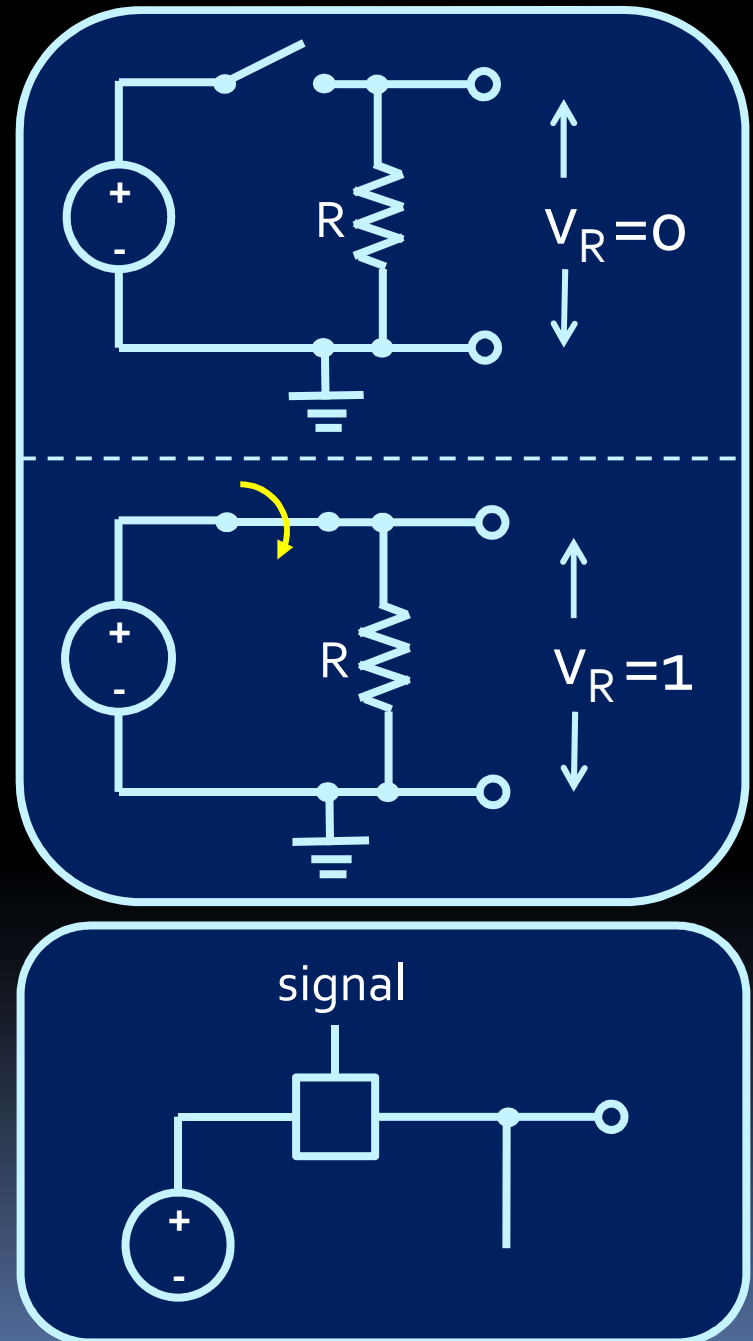
# What are gates?


- Gates are like switches, which control whether an output wire will have a high value (5V) or a low value (0V)
  - **Switches** are physical devices for manually closing a circuit.
  - **Gates** are semiconductor devices that close a circuit electrically.



# What are circuits?

- Assuming that certain signals can be turned on (one) or off (zero), we need have ways to combine these signals together.
  - Example #1: If the Ctrl, Alt and Delete buttons are being pressed, restart the computer.
  - Example #2: If three train tracks converge onto a single track, only turn on the green light if a single track has a train waiting.
- Every electronic device uses gates to combine input signals to create output signals.
- Very similar to CSC165 problems, but in hardware.



# Example: Ctrl-Alt-Delete

 

Ctrl	Alt	Del	RESTART
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1
  
# Expressing digital logic

- Given a logic problem or circuit, truth tables are used to describe its behavior (as in CSC165).
- Sometimes illustrated using a **waveform**.




A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

# Digital logic tasks (e.g. Lab 0)

- Given a truth table or circuit description, determine the circuit that creates it.
- Look at the conditions that cause high output signals.
- Express the high conditions as a boolean statement, then convert this to gates.

A	B	C	MOVE
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

# The course at a glance

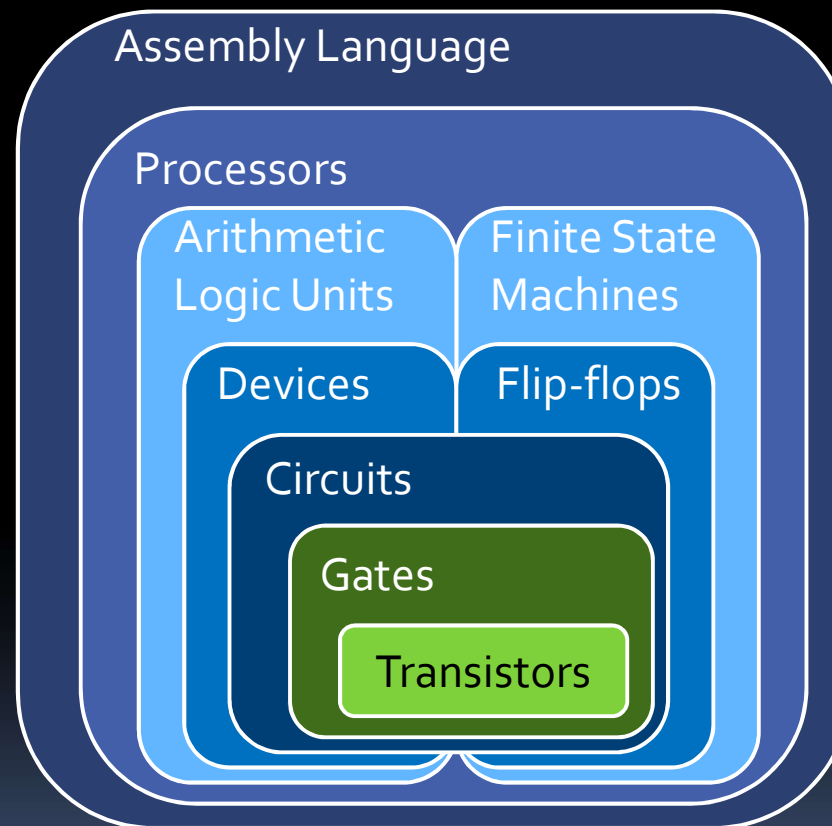



# Starting from the bottom

- Gates can combine values together like logical operators in C or Java.
- But how do gates work?
  - First, we need to understand electricity.
  - Then, we need to understand **transistors**.

